

## ACKNOWLEDGEMENT

By utilizing this website and/or documentation, I hereby acknowledge as follows:

Effective October 1, 2012, QUALCOMM Incorporated completed a corporate reorganization in which the assets of certain of its businesses and groups, as well as the stock of certain of its direct and indirect subsidiaries, were contributed to Qualcomm Technologies, Inc. (QTI), a wholly-owned subsidiary of QUALCOMM Incorporated that was created for purposes of the reorganization.

Qualcomm Technology Licensing (QTL), the Company's patent licensing business, continues to be operated by QUALCOMM Incorporated, which continues to own the vast majority of the Company's patent portfolio. Substantially all of the Company's products and services businesses, including QCT, as well as substantially all of the Company's engineering, research and development functions, are now operated by QTI and its direct and indirect subsidiaries<sup>1</sup>. Neither QTI nor any of its subsidiaries has any right, power or authority to grant any licenses or other rights under or to any patents owned by QUALCOMM Incorporated.

No use of this website and/or documentation, including but not limited to the downloading of any software, programs, manuals or other materials of any kind or nature whatsoever, and no purchase or use of any products or services, grants any licenses or other rights, of any kind or nature whatsoever, under or to any patents owned by QUALCOMM Incorporated or any of its subsidiaries. A separate patent license or other similar patent-related agreement from QUALCOMM Incorporated is needed to make, have made, use, sell, import and dispose of any products or services that would infringe any patent owned by QUALCOMM Incorporated in the absence of the grant by QUALCOMM Incorporated of a patent license or other applicable rights under such patent.

Any copyright notice referencing QUALCOMM Incorporated, Qualcomm Incorporated, QUALCOMM Inc., Qualcomm Inc., Qualcomm or similar designation, and which is associated with any of the products or services businesses or the engineering, research or development groups which are now operated by QTI and its direct and indirect subsidiaries, should properly reference, and shall be read to reference, QTI.

---

<sup>1</sup> The products and services businesses, and the engineering, research and development groups, which are now operated by QTI and its subsidiaries include, but are not limited to, QCT, Qualcomm Mobile & Computing (QMC), Qualcomm Atheros (QCA), Qualcomm Internet Services (QIS), Qualcomm Government Technologies (QGOV), Corporate Research & Development, Qualcomm Corporate Engineering Services (QCES), Office of the Chief Technology Officer (OCTO), Office of the Chief Scientist (OCS), Corporate Technical Advisory Group, Global Market Development (GMD), Global Business Operations (GBO), Qualcomm Ventures, Qualcomm Life (QLife), Quest, Qualcomm Labs (QLabs), Snaptracs/QCS, Firethorn, Qualcomm MEMS Technologies (QMT), Pixtronix, Qualcomm Innovation Center (QuIC), Qualcomm iSkoot, Qualcomm Poole and Xiam.



# ***Application Note***

---

## ***Battery Connection Transients***

**80-VC603-11 Rev. A**

**March 23, 2012**

---

**Submit technical questions at:**  
<https://support.cdmatech.com>

### **Qualcomm Confidential and Proprietary**

**Restricted Distribution.** Not to be distributed to anyone who is not an employee of either Qualcomm or a subsidiary of Qualcomm without the express approval of Qualcomm's Configuration Management.

Not to be used, copied, reproduced in whole or in part, nor its contents revealed in any manner to others without the express written permission of Qualcomm.

QUALCOMM is a registered trademark of QUALCOMM Incorporated in the United States and may be registered in other countries. Other product and brand names may be trademarks or registered trademarks of their respective owners. CDMA2000 is a registered certification mark of the Telecommunications Industry Association, used under license. ARM is a registered trademark of ARM Limited. QDSP is a registered trademark of QUALCOMM Incorporated in the United States and other countries.

This technical data may be subject to U.S. and international export, re-export, or transfer ("export") laws. Diversion contrary to U.S. and international law is strictly prohibited.

**QUALCOMM Incorporated  
5775 Morehouse Drive  
San Diego, CA 92121-1714  
U.S.A.**

**Copyright © 2012 QUALCOMM Incorporated.  
All rights reserved.**

## Revision history

Revision	Date	Description
A	March 2012	Initial release

QUALCOMM®  
2012.10.28 at 00:36:30 PDT  
linus.yue-zhntd.com

# 1 Introduction

When a battery is connected to a PMIC, the resulting transient voltage may propagate through the power management system and appear as a glitch on the supply voltages of circuits powered by the PMIC. Several points are worth emphasizing before presenting a more specific description:

- Connecting a battery to an actual product is a relatively rare occurrence.
  - Furthermore, the battery-connect transient does not cause an output glitch every time it is attached, making it even more rare.
- A smaller output glitch occurs when a charger (such as a USB or wall charger) is connected (a much more frequent event).
- The root cause is understood and is explained in [Chapter 2](#).
- Example scenarios, complete with representative voltage waveforms, are given in [Chapter 3](#).
- The slew rate of the battery-connect transient is an important aspect of this phenomenon (as demonstrated in [Chapter 3](#)).
  - A fast slew rate (high voltage change versus time) creates more severe output glitches.
  - A slow slew rate (low voltage change versus time) creates insignificant output glitches.
- Three factory test workarounds are available for eliminating or minimizing the output glitch generated by existing PMICs (all three are described further in [Section 4.1](#)):
  - The output glitch is not created when a battery is connected after a valid charger has established the primary phone power (VPH\_PWR or VDD).
  - The output glitch is limited using a two-step voltage initialization: (1) start the supply voltage at 1.8 V and (2) allow dVdd to settle. Any output glitches that might occur will be limited to less than 1.8 V. After a slight delay, change the supply voltage to its desired (final) setting.
  - The output glitch is minimized when a discharged battery is connected. This method might be particularly useful for products that include an embedded battery.
- All affected PMIC designs will be updated to prevent glitches from appearing on any circuit supply voltages generated by the PMIC. This is the identified final solution, as described in [Section 4.2](#).

## 1.1 Intended audience

This application note is intended for design and development engineering teams that create wireless products utilizing Qualcomm chipsets.

## 2 Problem Description

When a battery is attached to the product's PCB, a power supply transient is created that might propagate through the PMIC to other circuits that are powered by the PMIC. A high-level diagram of the propagation path is shown and explained in [Figure 1](#).


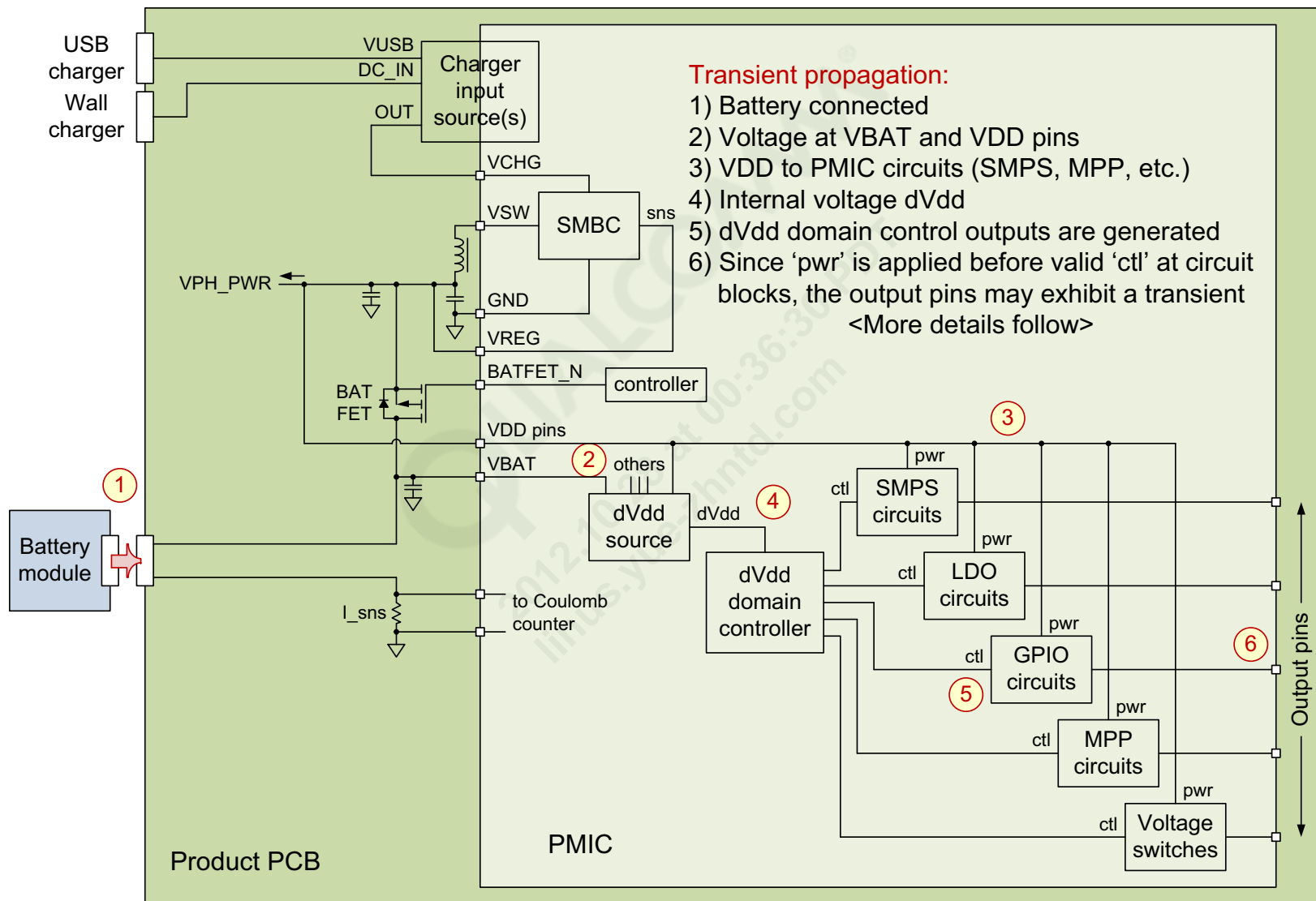



Figure 1 Power transient propagation path

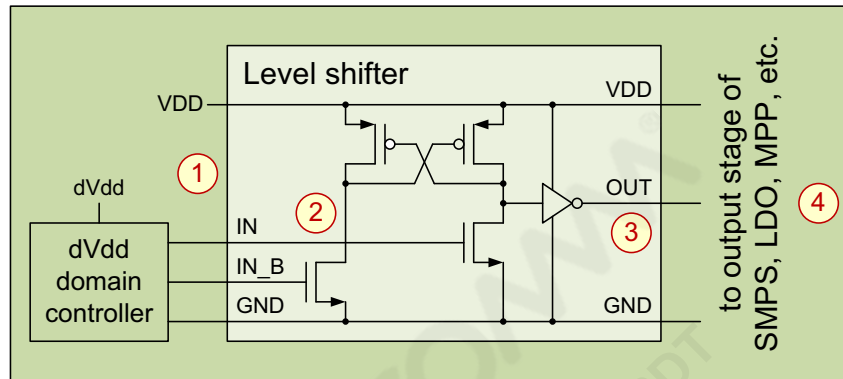The root cause of the output glitch is the undefined states of PMIC level shifter circuits (as explained in [Figure 2](#)). The PMIC circuits controlled by the level shifter outputs include, but are not limited to, SMPS and MPP circuits; these two circuits are described further in [Chapter 3](#) as example scenarios.



#### Uncertainty at level shifter:

- 1) VDD is applied before the dVdd domain controller outputs are valid
- 2) Undefined levels at IN and IN\_B ...
- 3) ... cause undefined level at OUT
- 4) Circuits being controlled by OUT have undefined inputs  
< see SMPS and MPP examples that follow >

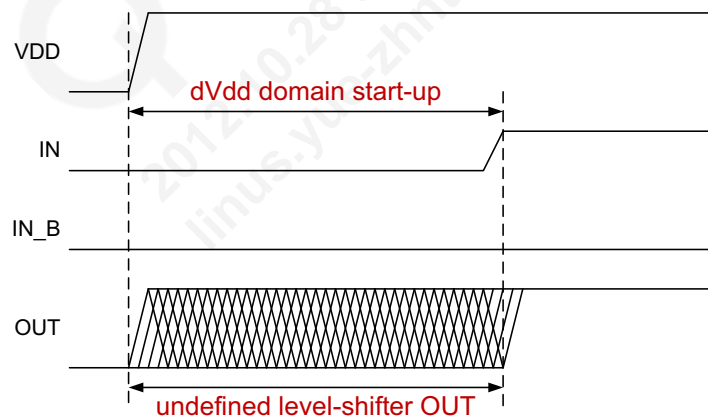

**Figure 2** Level shifter temporarily undefined inputs and outputs

### 3 Example Scenarios and Voltage Waveforms

Before presenting the SMPS and MPP circuits as examples, example waveforms showing the input voltage (VDD) and output glitches explained in [Section 3.1](#).

#### 3.1 Example voltage waveform


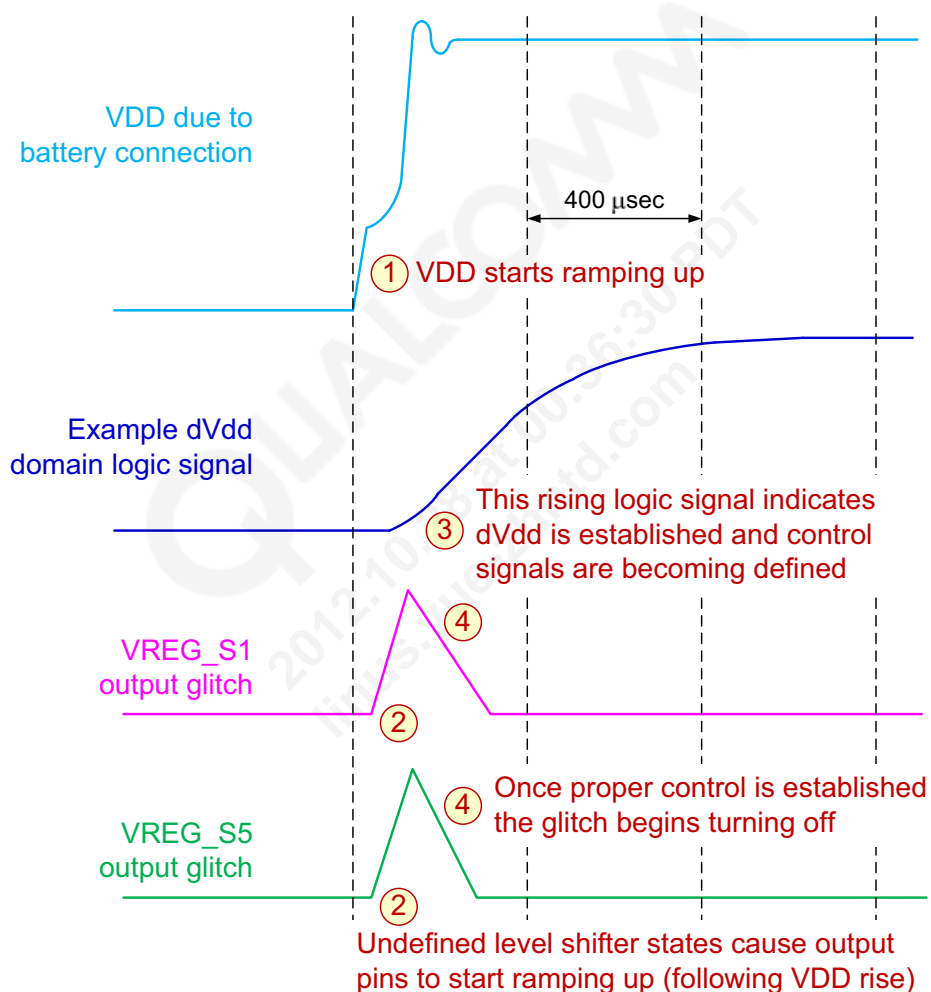


Figure 3 Example VDD input and output glitch waveforms

## 3.2 SMPS example

Temporary unknown  
control state ...

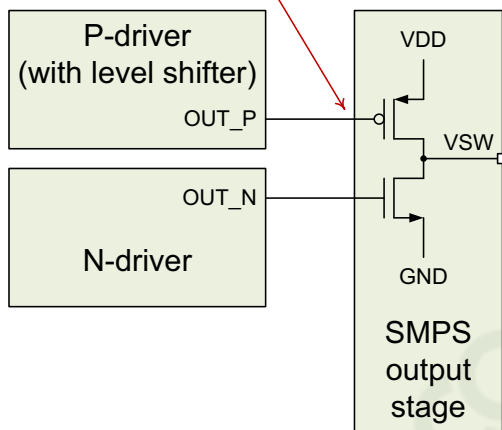

... could cause temporary VSW connection to  
VDD – the output follows VDD and creates glitch


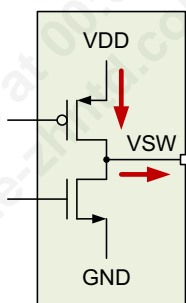


Figure 4 Example 1 – SMPS circuit

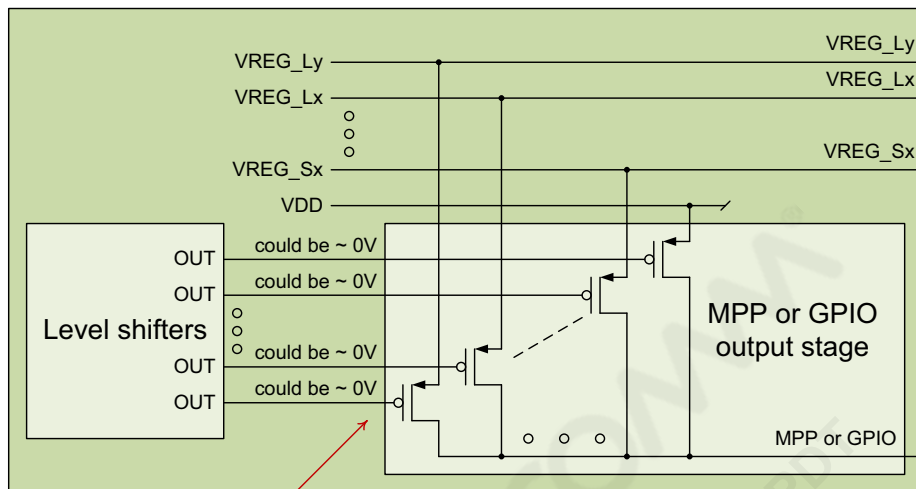

### 3.3 MPP example



Until dVdd domain  
output settles high ...

... multiple output voltage select  
switches can be on temporarily

If the VDD switch is on, VDD is connected  
directly to the output pin, and indirectly to any  
regulator output pin whose selection switch is on.

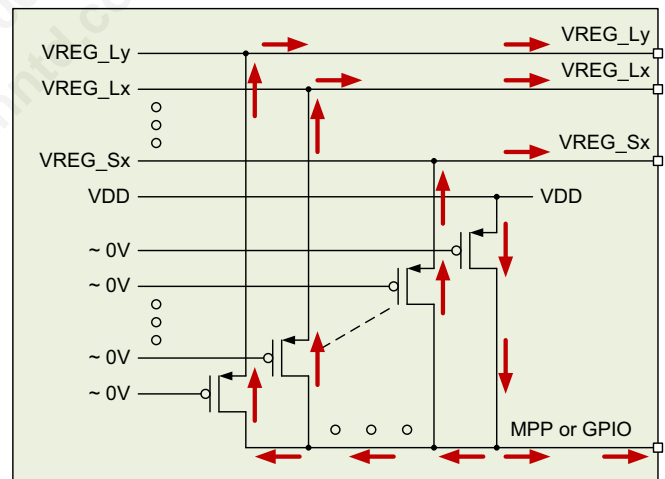


Figure 5 Example 2 – MPP leakage path to VREG outputs

### 3.4 Battery-connect VDD slew rate

Figure 6, shows how a slow slew rate prevents the battery-connect transient from generating a high output voltage. The interval during which the output stage is tracking VDD occurs when VDD is too low to be of any significant concern. The dVdd logic is established and turns off the output before its voltage rises too high.

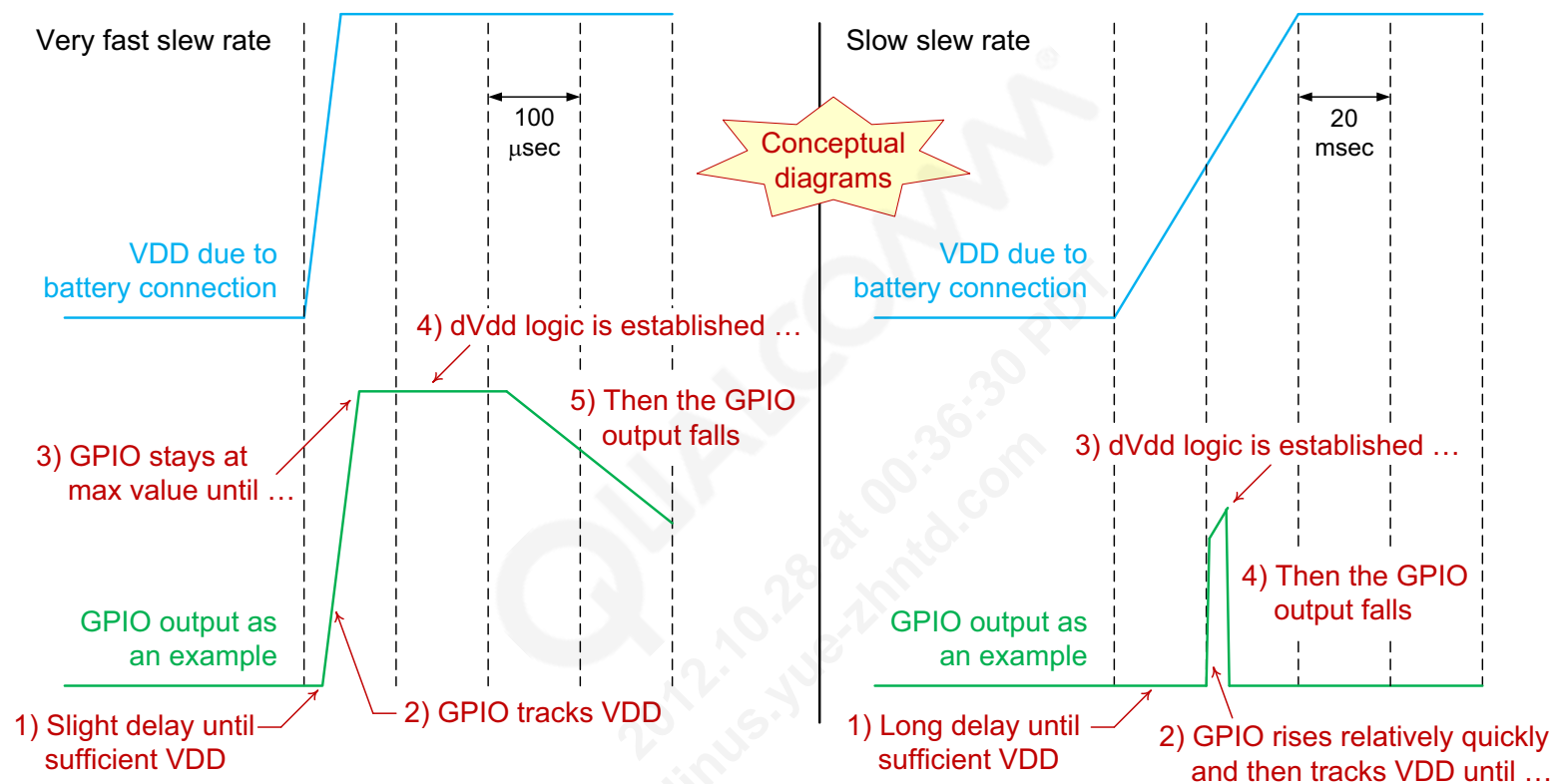


Figure 6 Battery-connect VDD slew rate

## 4 Solutions

There are two possible solutions:

1. Factory techniques that can be used immediately ([Section 4.1](#)) – techniques that avoid the battery-connect transient during factory testing.
2. The long-term, final solution ([Section 4.2](#)) that will eliminate the battery-connect transients entirely from future PMICs.

### 4.1 Factory testing of products using existing PMICs

Either of three recommended solutions can be used for near-term factory testing:

1. Connect an external charger

With an external charger connected (USB or wall charger), the SMBC circuit generates the VPH\_PWR voltage, and that voltage is used to establish the dVdd domain. The corresponding functional block diagram is included within [Figure 1](#). Connecting a battery after the dVdd domain is established (via the charger) does not generate glitches at any PMIC output pins.

2. Use a two-step voltage initialization

Start the supply voltage at 1.8 V and allow dVdd to settle. Any output glitches that might occur will be limited to less than 1.8 V. After a slight delay, change the supply voltage to its desired (final) setting. As stated in solution 1 above, connecting a battery after the dVdd domain is established does not generate glitches at any PMIC output pins.

This solution can be used whether the PMIC includes an integrated charger or not.

3. Discharged the embedded battery

If the product undergoing testing includes an embedded battery, that battery should be discharged before being installed. The output glitch is still created; however, it is minimized because the VDD level, while dVdd is being established, is too low to be a concern.

### 4.2 Final solution for all products using future PMICs

All affected PMIC designs will be updated to prevent glitches from appearing on any circuit supply voltages being generated by the PMIC. Elements of the solution include:

- The level shifter designs within circuits of concern (SMPS, LDO, MPP, GPIO, and voltage switches) are changed such that the internal dVdd domain must be established before those level shifters are enabled.
- The internal dVdd voltage is monitored; when dVdd is on and stable, a level shifter ‘enable’ signal is generated and routed to the level shifter circuits.